CIRCUIT DIAGRAM

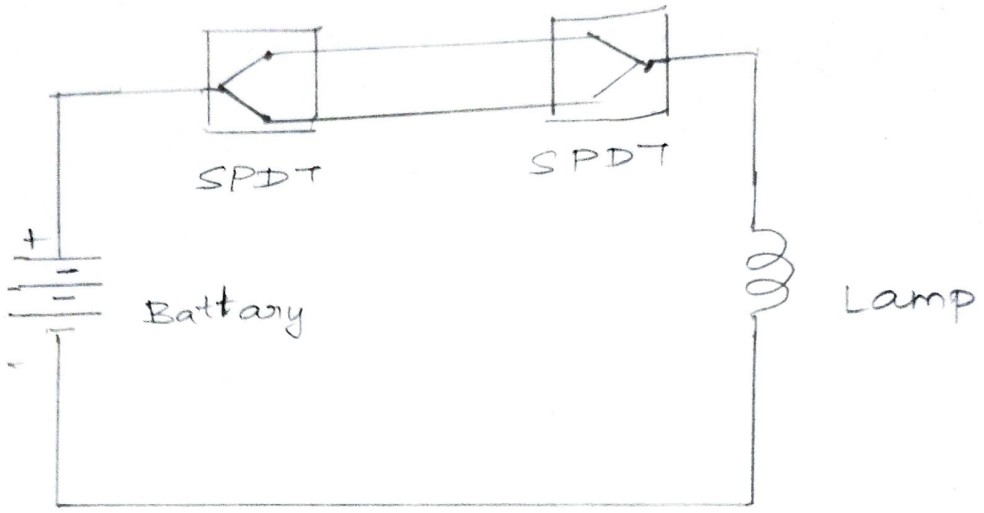

SPDT - Single pole double throw switch.

Mode	S_1	S_2	Lamp
1	ON	ON	ON
2	ON	OFF	OFF
3	OFF	ON	OFF
4	OFF	OFF	ON

STAIRCASE WIRING

AIM:

To develop and test the staircase wiring using proteus

APPARATUS REQUIRED:

Laptop with proteus Software

THEORY:

Staircase wiring is a common multiple way switching or two way switching connection. It involves wiring for one light with two switches. In this set up is controlled by two switches located operator the load. from separate position above or below the staircase from inside or outside of room or two way led switch.

CIRCUIT DIAGRAM :

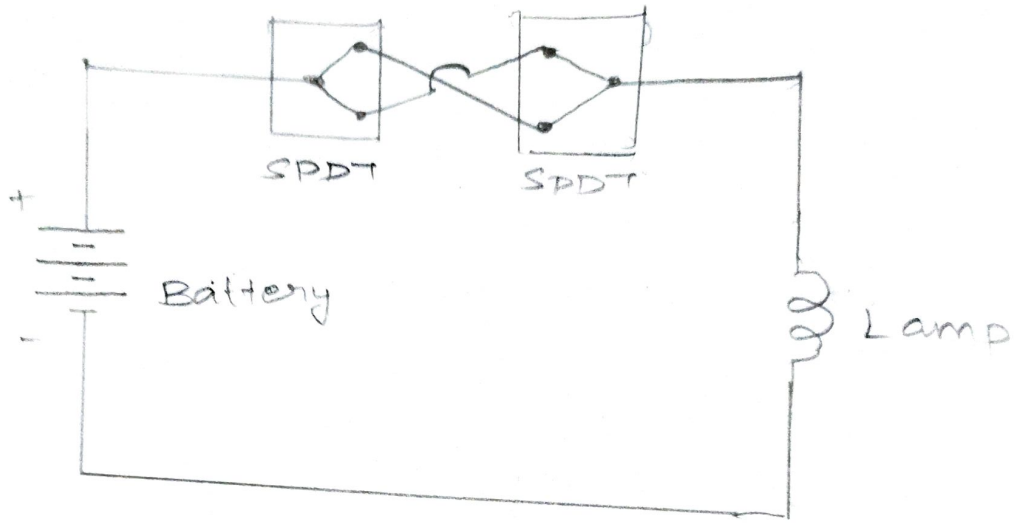

Mode	S_1	S_2	Lamp
1	ON	ON	OFF
2	ON	OFF	ON
3	OFF	ON	ON
4	OFF	OFF	OFF

PROCEDURE :

- Drag the required components from the process library.
- Connect the components as per circuit diagram.
- Run the simulation and check the lamp for different switching condition.

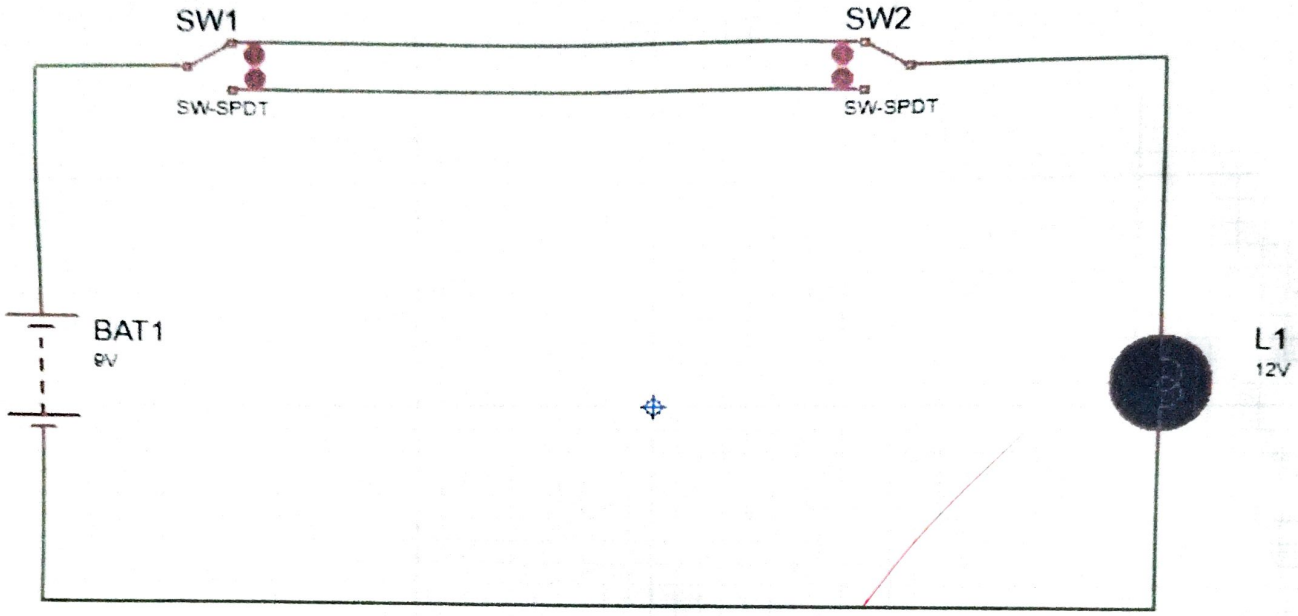
SW1
SW-SPDT
SW2
SW-SPDT
BAT1
9V
L1
12V

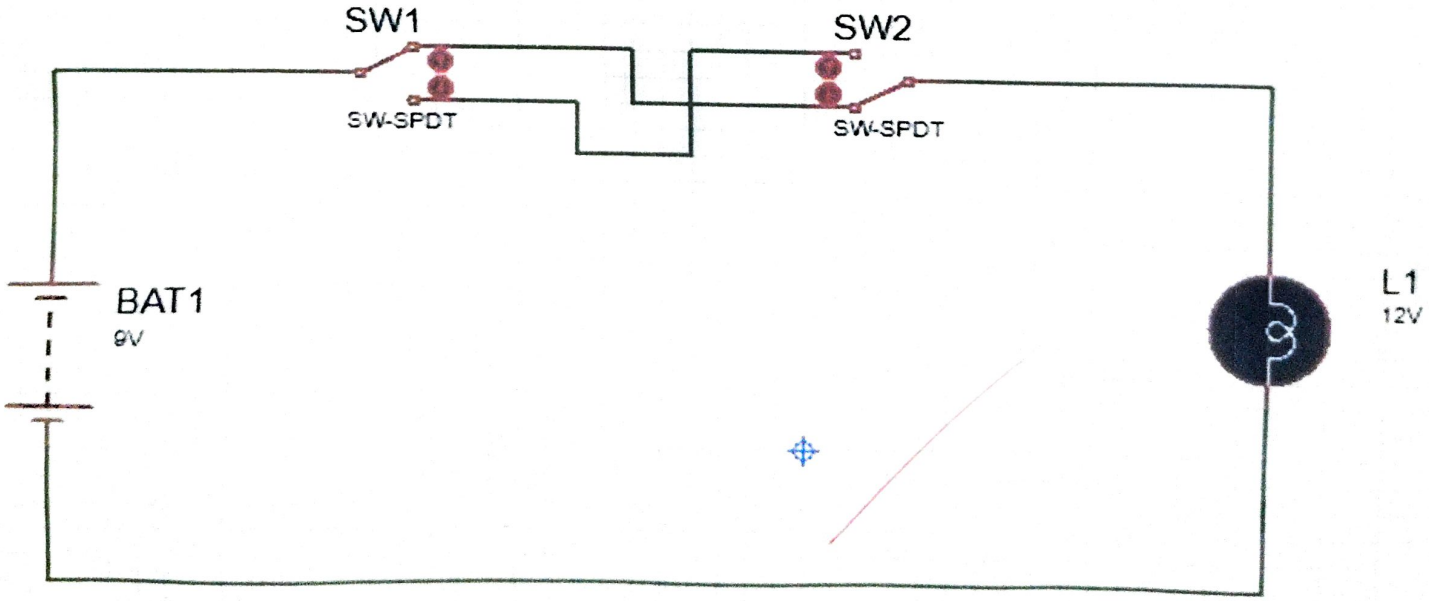
SW1
SW-SPDT
SW2
SW-SPDT
BAT1
9V
L1
12V

99

20/03/26

RESULT :

Thus, the staircase using connection were developed and tested successfully.